

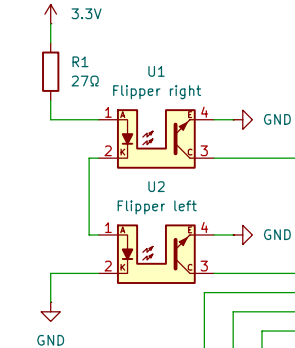


Light barrier TCST2103

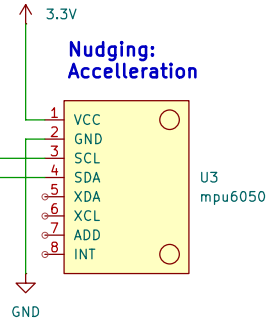Power supplies for the sender diodes are chained with the resistor R1 to get the needed voltage according the datasheet. Supply voltage is 1.25V (regular) up to 1.6V (max). The current should be about 20mA. With $270\Omega \cdot 0.02A = 0.54V$. Each Diode gets $(3.3V - 0.54V) / 2 = 1.38V$.




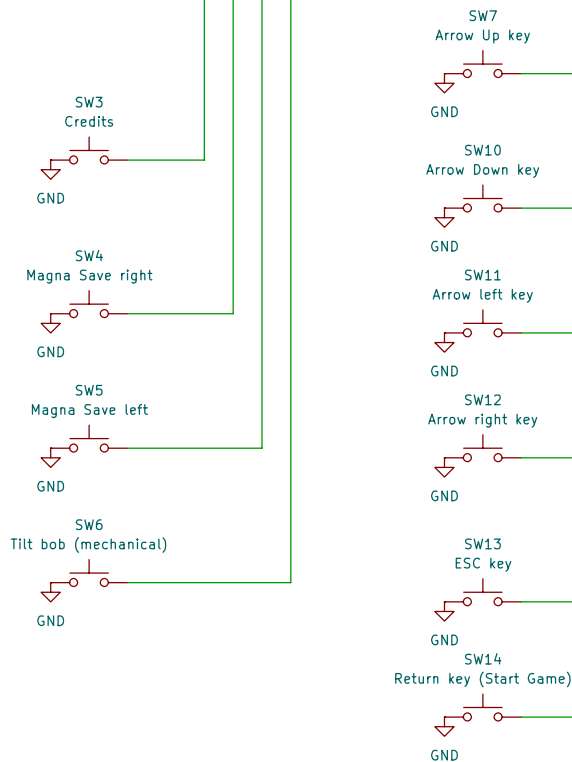The Flipper buttons can be done with mechanical barriers instead of light barriers. (i.e. arcade buttons) I just liked the idea of using light barriers.



Nudging:
Acceleration

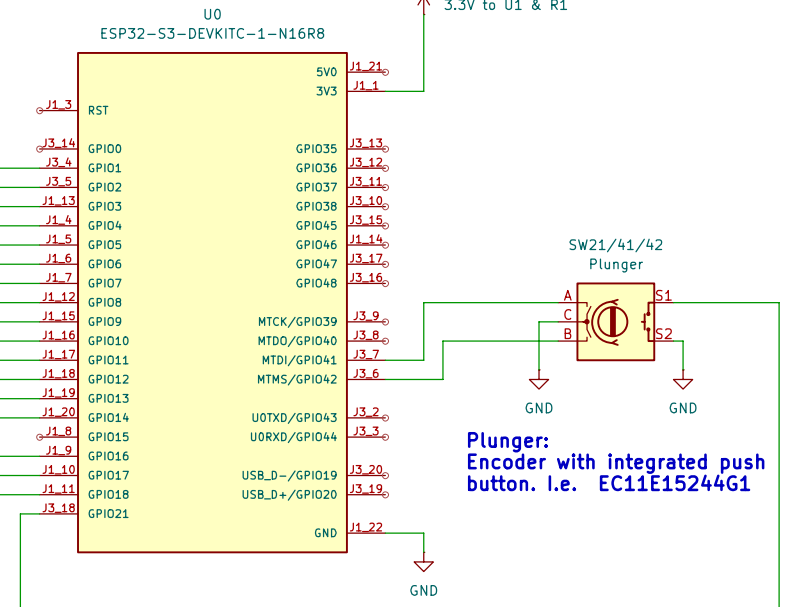Controller ESP32-S3 DEVKIT-1-N8R2 OR ...N16R8
They differ in memory sizes only. Connected to PC by USB cable. Being programmed and for working as Keyboard and Joystick device. The controller gets the power through the USB cable from the PC.



Plunger:
Encoder with integrated push button. i.e. EC11E15244G1

The Onboard Neopixel LED is on GPIO48. It lights up each time on of the contacts is operated. It helps to debug malfunctions.

If you have the two USB connectors against you... The controller needs to be loaded through the right plug. The USB keyboard- and joy stick functionality is given through the left plug.

FLIPerator Version 5: 08.12.2025
Switched the controller from Teensy 3.2 to ESP32-S3.